

CUET 2026 May 29 Shift 2 Physics

Question Paper (Memory-Based) with Solutions


Conducted by National Testing Agency (NTA)



General Instructions

- (i) The examination will be conducted in Computer-Based Test (CBT) mode.
- (ii) Each question carries +5 marks for correct answer and -1 mark for wrong answer.
- (iii) The total number of questions are 50.
- (iv) Duration of the exam is 1 hour (60 minutes).

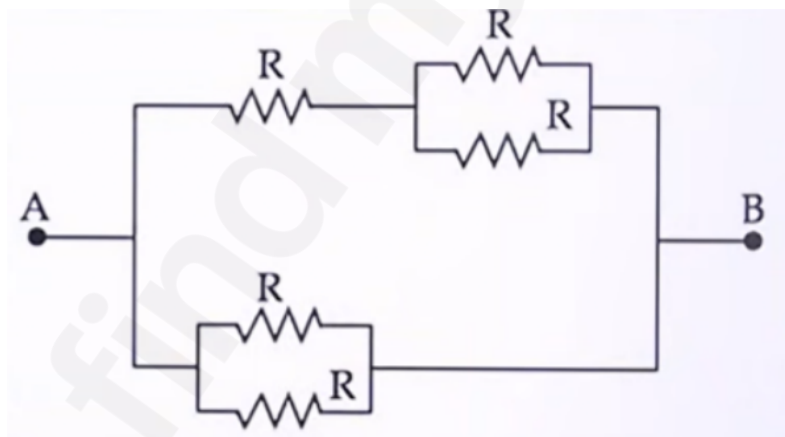1. Five resistors, each of resistance R , are connected between points A and B as shown in the figure. The equivalent resistance between A and B is:



- (A) $\frac{3R}{8}$
- (B) $5R$
- (C) $\frac{8R}{3}$
- (D) $2R$

Correct Answer: (A) $\frac{3R}{8}$

Solution:

Step 1: Simplify the upper branch.

In the upper branch, one resistor R is in series with two resistors R connected in parallel. The parallel combination is:

$$R_p = \frac{R \cdot R}{R + R} = \frac{R}{2}$$

Therefore, the equivalent resistance of the upper branch is:

$$R_{\text{upper}} = R + \frac{R}{2} = \frac{3R}{2}$$

Step 2: Simplify the lower branch.

The lower branch consists of two resistors R connected in parallel. Thus,

$$R_{\text{lower}} = \frac{R \cdot R}{R + R} = \frac{R}{2}$$

Step 3: Combine the two branches.

The upper and lower branches are connected in parallel between A and B. Hence,

$$\begin{aligned} R_{\text{eq}} &= \frac{R_{\text{upper}} R_{\text{lower}}}{R_{\text{upper}} + R_{\text{lower}}} \\ &= \frac{\left(\frac{3R}{2}\right)\left(\frac{R}{2}\right)}{\frac{3R}{2} + \frac{R}{2}} \\ &= \frac{\frac{3R^2}{4}}{2R} \\ &= \frac{3R}{8} \end{aligned}$$

Therefore,

$$\boxed{R_{\text{eq}} = \frac{3R}{8}}$$

Hence, the correct answer is:

(A)


Quick Tip: For two equal resistors R in parallel:

$$R \parallel R = \frac{R}{2}$$

A useful strategy for complex resistor networks is:

Simplify small parallel groups first, then combine series and parallel branches.

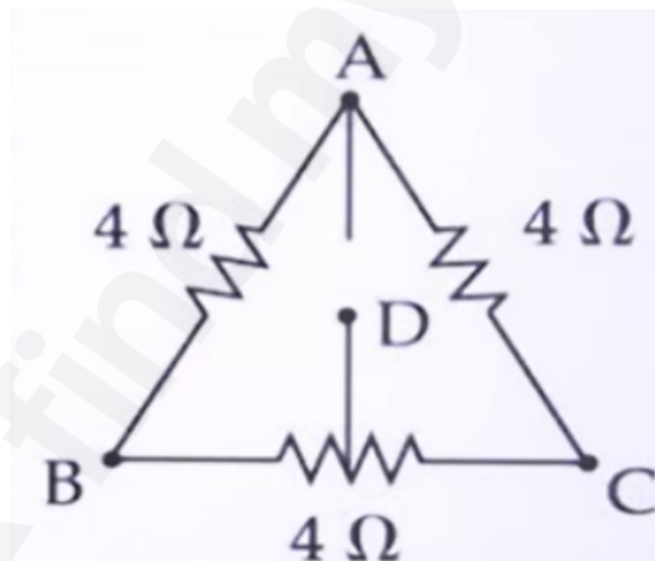2. In the figure shown, three resistors of 4Ω are connected. If point D divides the resistor between B and C into two equal parts, then the equivalent resistance between points A and D is:



- (A) 12Ω
- (B) 6Ω
- (C) 3Ω
- (D) $\frac{1}{3}\Omega$

Correct Answer: (C) 3Ω

Solution:

Step 1: Identify the resistance values.

Each side of the triangle has resistance

$$4\Omega$$

Since D is the midpoint of the resistor BC ,

$$BD = DC = 2\Omega$$

Step 2: Find the two paths between A and D .

Path 1:

$$A \rightarrow B \rightarrow D$$

Resistance along this path:

$$R_1 = 4 + 2 = 6\Omega$$

Path 2:

$$A \rightarrow C \rightarrow D$$

Resistance along this path:

$$R_2 = 4 + 2 = 6\Omega$$

Step 3: Combine the two paths.

The two 6Ω paths are connected in parallel between A and D .

Therefore,

$$R_{AD} = \frac{6 \times 6}{6 + 6}$$

$$= \frac{36}{12}$$

- (B) 18Ω
 (C) 4Ω
 (D) 14Ω

Correct Answer: (B) 18Ω

Solution:

Step 1: Analyze the upper triangular section.

Between the two upper junctions, there are two possible paths:

Direct path:

$$8\Omega$$

Upper path through the apex:

$$4 + 4 = 8\Omega$$

Therefore these two 8Ω resistances are in parallel.

$$R_{\text{upper}} = 8 \parallel 8 = \frac{8 \times 8}{8 + 8} = 4\Omega$$

Step 2: Replace the upper section.

The circuit now becomes a rectangle with:

$$4\Omega$$

between the upper junctions and

$$12\Omega$$

between the lower junctions.

The side resistances are:

$$4\Omega$$

on the left and

$$4\Omega$$

on the right.

Step 3: Find equivalent resistance between the lower junctions.

One path is directly:

$$12\Omega$$

The other path goes through the upper branch:

$$4 + 4 + 4 = 12\Omega$$

Hence,

$$R = 12 \parallel 12 = 6\Omega$$

Step 4: Include the terminal resistors.

The 6Ω resistor from A to the left junction and the 6Ω resistor from the right junction to B are in series with the equivalent found above.

Thus,

$$R_{AB} = 6 + 6 + 6$$

$$R_{AB} = 18\Omega$$

Therefore,

$$R_{AB} = 18\Omega$$

Hence, the correct answer is:

(B)

Quick Tip: Whenever a triangular resistor network contains:

$$R \text{ in parallel with } (R_1 + R_2),$$


reduce that section first.

Here:

$$8\Omega \parallel (4\Omega + 4\Omega) = 8\Omega \parallel 8\Omega = 4\Omega$$

After simplification, the remaining network becomes a simple series-parallel combination.

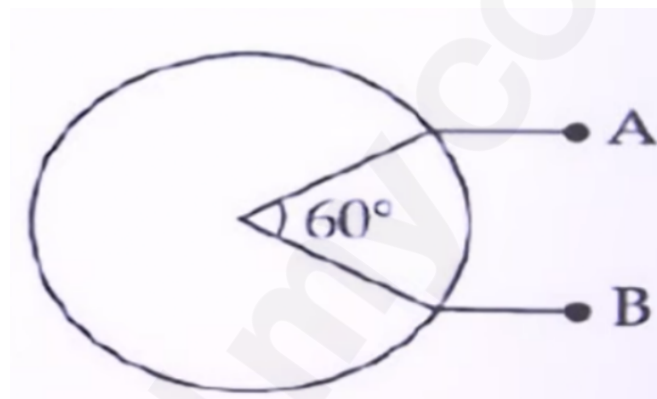4. A wire of uniform cross-sectional area and resistivity has total resistance 36Ω and is bent into a circle as shown in the figure. The equivalent resistance between points A and B is:



- (A) 6Ω
- (B) 5Ω
- (C) 30Ω
- (D) 42Ω

Correct Answer: (B) 5Ω

Solution:

Step 1: Determine the resistances of the two arcs.

The wire forms a complete circle of total resistance:

$$R = 36\Omega$$

The points A and B subtend an angle of

$$60^\circ$$

Therefore, resistance of the smaller arc is:

$$R_1 = 36 \left(\frac{60}{360} \right) = 6 \Omega$$

The remaining arc subtends

$$360^\circ - 60^\circ = 300^\circ$$

Hence,

$$R_2 = 36 \left(\frac{300}{360} \right) = 30 \Omega$$

Step 2: Identify the combination.

The two arcs connect the same points A and B.

Therefore, they are in parallel.

$$R_{AB} = \frac{R_1 R_2}{R_1 + R_2}$$

$$= \frac{(6)(30)}{6 + 30}$$

$$= \frac{180}{36}$$

$$= 5 \Omega$$

Step 3: Identify the correct option.

$$\boxed{R_{AB} = 5 \Omega}$$

Hence, the correct answer is:

(B)

Quick Tip: For a circular wire of total resistance R :

$$R_{\text{arc}} = R \left(\frac{\theta}{360^\circ} \right)$$

If two arcs connect the same terminals, they are in parallel.


For an angle θ :

$$R_1 = \frac{\theta}{360^\circ} R, \quad R_2 = \frac{360^\circ - \theta}{360^\circ} R$$

and

$$R_{\text{eq}} = \frac{R_1 R_2}{R_1 + R_2}$$

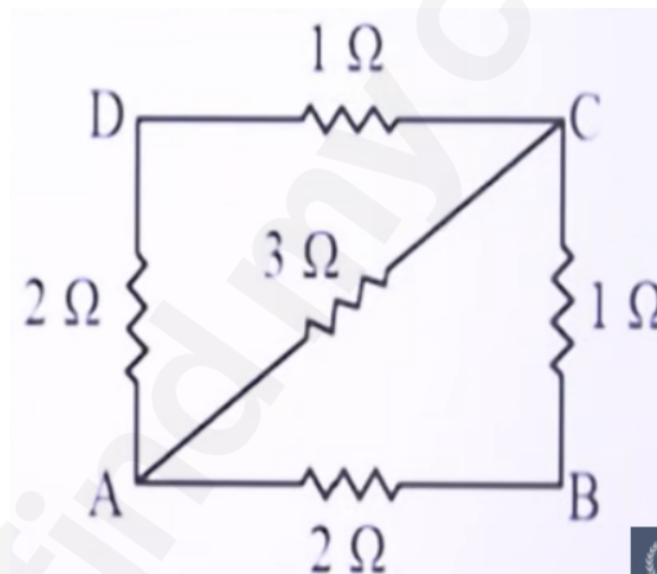5. The equivalent resistance of the following combination of resistances between A and C is:



- (A) 36Ω
- (B) 1Ω
- (C) 27Ω
- (D) 3Ω

Correct Answer: (B) 1Ω

Solution:

Step 1: Identify the three paths between A and C .

Upper path:

$$A \rightarrow D \rightarrow C$$

Resistance:

$$R_1 = 2 + 1 = 3 \Omega$$

Lower path:

$$A \rightarrow B \rightarrow C$$

Resistance:

$$R_2 = 2 + 1 = 3 \Omega$$

Diagonal path:

$$A \rightarrow C$$

Resistance:

$$R_3 = 3 \Omega$$

Step 2: Observe the parallel combination.

All three branches connect directly between the same terminals A and C .

Hence the three 3Ω resistors are in parallel.

$$\frac{1}{R_{eq}} = \frac{1}{3} + \frac{1}{3} + \frac{1}{3}$$

$$\frac{1}{R_{eq}} = 1$$

Therefore,

$$R_{eq} = 1 \Omega$$

Step 3: Select the correct option.

$$R_{\text{eq}} = 1 \Omega$$

Hence, the correct answer is:

(B)

Quick Tip: If n equal resistors of resistance R are connected in parallel:

$$R_{\text{eq}} = \frac{R}{n}$$

Here,

$$3\Omega \parallel 3\Omega \parallel 3\Omega = \frac{3}{3} = 1\Omega$$

Always look for complete paths joining the same two terminals before simplifying a resistor network.

6. A straight wire of mass 200 g and length 1.5 m carries a current of 2 A. It is suspended in mid-air by a uniform horizontal magnetic field B . The magnitude of B is ($g = 10 \text{ m s}^{-2}$):

- (A) 2 T
- (B) 1.5 T
- (C) 0.55 T
- (D) 0.67 T

Correct Answer: (D) 0.67 T

Solution:

Step 1: Apply the condition for suspension.

For the wire to remain suspended in air, the magnetic force must balance its weight.

$$F_B = mg$$

Step 2: Use magnetic force on a current-carrying conductor.

The magnetic force is given by:

$$F_B = BIL \sin \theta$$

For maximum upward force,

$$\theta = 90^\circ$$

Therefore,

$$F_B = BIL$$

Step 3: Substitute the given values.

Mass:

$$m = 200 \text{ g} = 0.2 \text{ kg}$$

Weight:

$$mg = 0.2 \times 10 = 2 \text{ N}$$

Using

$$BIL = mg$$

$$B \times 2 \times 1.5 = 2$$

$$3B = 2$$

$$B = \frac{2}{3} \text{ T}$$

$$B = 0.67 \text{ T}$$

Therefore,

$$B = 0.67 \text{ T}$$

Hence, the correct answer is:

(D)

Quick Tip: For a current-carrying wire suspended by a magnetic field:

$$BIL = mg$$

Hence,

$$B = \frac{mg}{IL}$$

This formula is frequently asked in CUET, JEE Main and NEET Physics examinations.

7. A straight wire of mass 500 g and length 7 m carries a current of 1.4 A. It is suspended in mid-air by a uniform horizontal magnetic field B perpendicular to the length of the wire. The magnitude of the magnetic field is:

- (A) 3.5 T
- (B) 0.7 T
- (C) 0.5 T
- (D) 2.5 T

Correct Answer: (C) 0.5 T

Solution:

Step 1: Apply the condition for suspension.

Since the wire is suspended in air, the magnetic force balances its weight.

$$F_B = mg$$

Step 2: Use the magnetic force formula.

Magnetic force on a current-carrying conductor is:

$$F_B = BIL \sin \theta$$

Since the magnetic field is perpendicular to the wire,

$$\theta = 90^\circ$$

and therefore,

$$F_B = BIL$$

Step 3: Substitute the given values.

$$m = 500 \text{ g} = 0.5 \text{ kg}$$

Taking

$$g = 9.8 \text{ m s}^{-2}$$

$$mg = 0.5 \times 9.8 = 4.9 \text{ N}$$

Using

$$BIL = mg$$

$$B \times 1.4 \times 7 = 4.9$$

$$9.8B = 4.9$$

$$B = \frac{4.9}{9.8}$$

$$B = 0.5 \text{ T}$$

Therefore,

$$B = 0.5 \text{ T}$$

Hence, the correct answer is:

(C)

Quick Tip: For a wire suspended by magnetic force:

$$BIL = mg$$

Hence,

$$B = \frac{mg}{IL}$$

When the magnetic field is perpendicular to the wire,

$$\sin 90^\circ = 1$$

which gives the maximum magnetic force.

8. If a straight wire of length 175 cm and mass 250 g is suspended freely in a uniform horizontal magnetic field of 0.7 T, then the current flowing through the wire is:

- (A) 20 A
- (B) 0.02 A
- (C) 2 A
- (D) 0.2 A

Correct Answer: (C) 2 A

Solution:

Step 1: Apply the condition for suspension.

For the wire to remain suspended,

$$F_B = mg$$

Step 2: Use the magnetic force formula.

Magnetic force on a current-carrying conductor is:

$$F_B = BIL \sin \theta$$

For maximum upward force,

$$\theta = 90^\circ$$

Thus,

$$BIL = mg$$

Step 3: Substitute the given values.

$$m = 250 \text{ g} = 0.25 \text{ kg}$$

$$L = 175 \text{ cm} = 1.75 \text{ m}$$

$$B = 0.7 \text{ T}$$

Taking

$$g = 9.8 \text{ m s}^{-2}$$

$$I = \frac{mg}{BL}$$

$$I = \frac{0.25 \times 9.8}{0.7 \times 1.75}$$

$$I = \frac{2.45}{1.225}$$

$$I = 2 \text{ A}$$

Therefore,

$$I = 2 \text{ A}$$

Hence, the correct answer is:

(C)

Quick Tip: For a wire suspended by magnetic force:

$$BIL = mg$$

Hence,

$$I = \frac{mg}{BL}$$

Always convert:


$$\text{cm} \rightarrow \text{m}$$

and

$$g \rightarrow \text{kg}$$

before substitution.

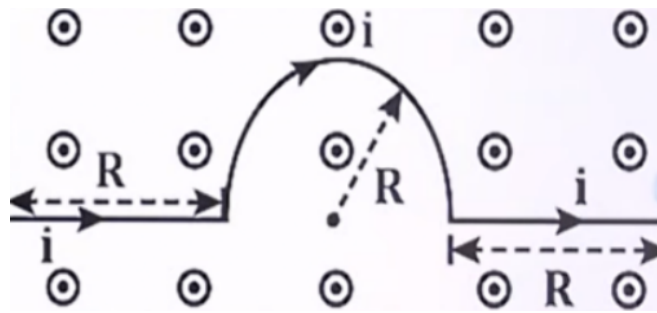9. A wire carrying current i , bent as shown in the figure, is placed in a uniform magnetic field B directed normally out of the plane of the figure. The force on the wire is:



- (A) $4BiR$, directed vertically downward
 (B) $3BiR$, directed vertically upward
 (C) $Bi(2R + \pi R)$, directed vertically downward
 (D) $2BiR$, from P to Q

Correct Answer: (A) $4BiR$, directed vertically downward

Solution:

Step 1: Use the force formula for a wire in a uniform magnetic field.

For a wire carrying current in a uniform magnetic field,

$$\vec{F} = I \int d\vec{l} \times \vec{B}$$

Since $\vec{B}$ is uniform,

$$\vec{F} = I(\vec{L}) \times \vec{B}$$

where $\vec{L}$ is the displacement vector joining the initial and final points of the wire.

Step 2: Find the effective displacement.

The wire consists of:

- Left straight segment of length R
- Semicircular arc of radius R
- Right straight segment of length R

The horizontal displacement between the two end points is

$$R + 2R + R = 4R$$

Thus,

$$L = 4R$$

directed horizontally.

Step 3: Calculate the magnitude of force.

Since $\vec{L}$ lies in the plane of the paper and $\vec{B}$ is perpendicular to the plane,

$$\theta = 90^\circ$$

Therefore,

$$F = BIL \sin 90^\circ$$

$$F = BI(4R)$$

$$F = 4BiR$$

Step 4: Determine the direction.

Current flows from left to right and magnetic field is out of the plane.

Using the right-hand rule:

$$\vec{F} = \vec{L} \times \vec{B}$$

the force acts vertically downward.

Therefore,

$$F = 4BiR$$

directed vertically downward.

Hence, the correct answer is:

$$(A)$$

Quick Tip: For any shaped wire placed in a **uniform** magnetic field,

$$\vec{F} = I (\vec{r}_{\text{final}} - \vec{r}_{\text{initial}}) \times \vec{B}$$

The force depends only on the displacement between the endpoints, not on the actual shape of the wire.

This is a very common CUET/JEE conceptual question.

10. The most exotic diamagnetic materials are superconductors. They exhibit perfect diamagnetism and perfect conductivity. The values of magnetic susceptibility (χ) and relative permeability (μ_r) for such materials are:

- (A) $\chi = 1, \mu_r = 0$
- (B) $\chi = -1, \mu_r = 0$
- (C) $\chi = 0, \mu_r = 1$
- (D) $\chi = -1, \mu_r = 1$

Correct Answer: (B) $\chi = -1, \mu_r = 0$

Solution:

Step 1: Recall the magnetic properties of superconductors.

A superconductor exhibits:

Perfect diamagnetism

This phenomenon is known as the

Meissner Effect

in which magnetic flux is completely expelled from the interior of the material.

Step 2: Find the magnetic susceptibility.

For a perfect diamagnetic substance,

$$\chi = -1$$

Step 3: Use the relation between permeability and susceptibility.

The relative permeability is related to susceptibility by

$$\mu_r = 1 + \chi$$

Substituting

$$\chi = -1$$

gives

$$\mu_r = 1 - 1$$

$$\mu_r = 0$$

Step 4: Identify the correct option.

Thus,

$$\chi = -1, \quad \mu_r = 0$$

Hence, the correct answer is:

(B)

Quick Tip: For superconductors:

$$\chi = -1$$

$$\mu_r = 0$$

because

$$\mu_r = 1 + \chi$$

The complete expulsion of magnetic field from a superconductor is called the

Meissner Effect

which is a favorite CUET/JEE conceptual question.